

Electrical Measurement


Kirchoff's law

- First law:**

In an electric circuit, the algebraic sum of currents at any junction point is zero. i.e. $\sum I = 0$ e.g. in figure a point A:

$$I_1 + I_5 + I_4 + I_3 - I_2 = 0$$

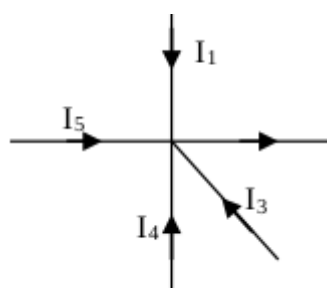
In this law the current flowing towards the points are taken +ve sign while the current flowing away from the point are taken -ve sign.



This law is based on law of conservation of charge.

- Second Law:**

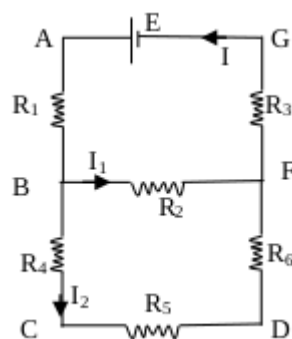In a closed circuit the algebraic sum of products of current and resistance is equal to the total emf in the circuit i.e. $\sum E = \sum IR$. This law is based on the law of conservation of energy.




In the circuit, in mesh BCDFB:

$$I_2 R_4 + I_2 R_5 + I_2 R_6 - I_1 R_2 = 0$$

$$\text{Or, } I_2 R_4 + I_2 R_5 + I_2 R_6 = I_1 R_2$$

The Kirchhoff's first law is applied at the junction so, called junction law & second law is used at loop (mesh) so called loop law.

Wheatstone's Bridge Network

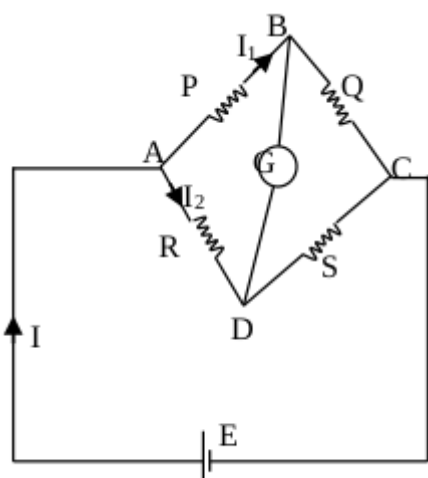

The Wheatstone's bridge is shown in figure P, Q, R and S are four resistances and E is a battery. The Wheatstone's bridge is said to be balanced when no current flows in galvanometer i.e. when potential of B = potential of D.

This condition of balanced Wheatstone's bridge is achieved, when

$$\frac{P}{Q} = \frac{R}{S} \Rightarrow QR = PS$$

Meter Bridge

Meter bridge works on the principle of Wheatstone's bridge and is used to determine the unknown resistance.

$$S = \frac{R(100 - l)}{l}$$

where,

S = unknown resistance

R = known resistance

l = balancing length

The bridge become most sensitive when all four resistors are of same order.

Potentiometer

A potentiometer generally consists of uniform wire of length 10m stretched on a wooden board between two thick copper strips. Each wire is 100 cm long. A meter scale is fitted parallel to its length. A steady current is set up in the wire by means of a battery. This maintains the uniform potential gradient along the length of wire.

i. Potential gradient,

$$\left(\frac{dV}{dl} \right) = \frac{V_A - V_B}{l} = \frac{P.D.}{\text{length of wire}}$$

ii. Comparison of emf,

$$\frac{E_1}{E_2} = \frac{I_1}{I_2}$$

iii. Internal resistance,

$$r = \left(\frac{l_1}{l_2} - 1 \right) R$$

where,


$R \rightarrow$ known resistance

$l_1 \rightarrow$ balance length for emf

$l_2 \rightarrow$ balance length for terminal p.d

Conversion of galvanometer into ammeter

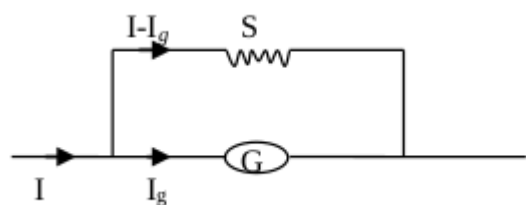A galvanometer of resistance G and full scale deflection current I_g converted into an ammeter of range $0 - I$ by shunting it with resistance S .




$$S = \frac{I_a}{I - I_g} G = \frac{G}{\left(\frac{I}{I_g} - 1 \right)} = \frac{G}{n - 1}$$

$$\text{where } n = \frac{I}{I_g}$$

$$\text{Total resistance of ammeter } (G') = \frac{SG}{S + G}$$

Conversion of galvanometer into voltmeter

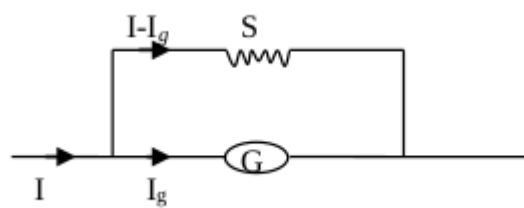A galvanometer of resistance G and full scale deflection current I_g is converted into a voltmeter of range $0 - V$ by connecting a resistance R in series.



$$R = \frac{V}{I_g} - G$$

Total resistance of voltmeter = $R + G$