

Alternating Current

Introduction

It is the current which varies continuously in magnitude and periodically reverse in direction.

- When a coil is rotated in magnetic field, an alternating e.m.f. is generated in the coil. At any instant, the emf is given by

$$E = E_0 \sin \omega t$$

where E_0 = peak emf or maximum emf

General equation of AC

$$V = V_0 \sin \omega t \quad \text{and} \quad I = I_0 \sin \omega t$$

$$V = V_0 \sin 2\pi ft \quad \text{and} \quad I = I_0 \sin 2\pi ft$$

- After starting from zero the time taken by current (or voltage) to reach maximum value is $T/4$.

Average value

Average value of AC for one complete cycle is zero.

Average value for half cycle:

$$I_{avg} = \frac{\int_0^{T/2} I \cdot dt}{\int_0^{T/2} dt}$$

For sinusoidal AC:

$$I_{av} = \frac{2I_0}{\pi} \quad \text{and} \quad V_{av} = \frac{2V_0}{\pi}$$

$$= 0.637I_0 = 63.7\% \text{ of } I_0$$

RMS value

$$I_{rms} = \frac{\int_0^T i^2 dt}{\int_0^T dt}$$

1. For sinusoidal AC:

$$I_{rms} = \frac{I_0}{\sqrt{2}} = 70.7\% \text{ of } I_0$$

$$V_{rms} = \frac{V_0}{\sqrt{2}} = 70.7\% \text{ of } V_0$$

2. If $I = I_1 \sin \omega t + \frac{I_2 \cos \omega t}{\sqrt{2}}$, then

$$I_{ms} = \frac{\sqrt{I_1^2 + \left(\frac{I_2}{\sqrt{2}}\right)^2}}{\sqrt{2}}$$

$$I_{max} = \sqrt{I_1^2 + \left(\frac{I_2}{\sqrt{2}}\right)^2}$$

$$I_{av} = \frac{2}{\pi} \sqrt{I_1^2 + \left(\frac{I_2}{\sqrt{2}}\right)^2}$$

3. If $I = I_1 \sin \omega t + I_2 \cos \omega t$

$$I_{max} = \sqrt{I_1^2 + I_2^2}$$

$$I_{rms} = \frac{\sqrt{I_1^2 + I_2^2}}{\sqrt{2}}$$

$$I_{av} = \frac{2}{\pi} \sqrt{I_1^2 + I_2^2}$$

- AC is measured by hot wire instrument.
- AC ammeter and voltmeter measures rms value.
- Hot wire meter reads both AC and DC.

- Moving coil ammeter is not used with AC circuit because average value is zero.
- In AC mains voltage 220 V represents rms value of supply.

$$V_{max} = V_0 = \sqrt{2} \text{ rms}$$
- Peak to peak voltage = $2V_0 = 2\sqrt{2} \text{ rms}$

Form factor

It is the ratio of rms value to average value.

For sine value:

Form factor = 1.11

Impedance (Z)

It is the total opposing resistance in an AC circuit.

$$Z = \frac{E_{rms}}{I_{rms}} = \frac{E_0}{I_0}$$

Inductive reactance

$$(X_L) = \omega L = 2\pi fL$$

$$\text{Capacitive reactance } (X_C) = \frac{1}{\omega C} = \frac{1}{2\pi fC}$$

Reactance (X): The hindrance offered by inductance and capacitance in an AC circuit.

Susceptance (S)

It is the reciprocal of reactance.

$$S = \frac{1}{X}; \quad S_L = \frac{1}{X_L}; \quad S_C = \frac{1}{X_C}$$

$$[S] = \text{M}^{-1} \text{L}^{-2} \text{T}^3 \text{A}^2$$

Admittance (γ)

It is the reciprocal of impedance.

$$\gamma = \frac{1}{Z}; \quad [\gamma] = \text{M}^{-1} \text{L}^2 \text{T}^3 \text{A}^2$$

- Power in AC circuit:
 $P = V_{rms} \times I_{rms} \times \cos\theta$; $\cos\theta$ is power factor.
- Power factor is defined as the ratio of true power to apparent power.

AC through pure resistor (R)

$$I = I_0 \sin \omega t; I = \frac{V_0}{R}$$

$$P_{av} = V_{rms} \times I_{rms} = I_{rms}^2 R = \frac{V_0 I_0}{2} = \frac{V_0^2}{2R}$$

- There is no leading and no lagging between current and voltage in pure resistance.
 $\theta = 0$
 Power factor, $\cos\theta = 1$

AC through pure inductor (L)

Inductive reactance; $X_L = \omega L = 2\pi fL$

$$\text{If } V = V_0 \sin \omega t, \text{ then } I = I_0 \sin\left(\omega t - \frac{\pi}{2}\right)$$

$$\theta = -\frac{\pi}{2}$$

$$I_0 = \frac{V_0}{X_L} = \frac{V_0}{2\pi fL}$$

- There is a phase difference of 90° produced between current and voltage.
- Current lags behind the voltage by $\pi/2$.
- For pure inductor, $\theta = \frac{\pi}{2}$; $\cos\theta = 0$
- Average power dissipation in pure inductor is zero.

AC through pure capacitance (C)

Capacitive reactance; $X_C = \omega C = \frac{1}{2\pi fC}$

If $V = V_0 \sin \omega t$, then, $I = I_0 \sin\left(\omega t + \frac{\pi}{2}\right)$

$$I_0 = \frac{V_0}{X_L} \quad \theta = +\frac{\pi}{2}; \cos \theta = 0$$

- Average power dissipation in pure capacitor is zero.
- Current leads the voltage by $\pi/2$.

AC with RC series circuit

Impedance:

$$Z = \sqrt{X_L^2 + R^2}; V = IZ$$

$$\cos \theta = \frac{R}{Z}$$

$$V = \sqrt{V_L^2 + V_R^2}$$

$$0 < \theta < \frac{\pi}{2}$$

AC with LR series circuit

$$X_L = \omega L = 2\pi fL$$

$$Z = \sqrt{R^2 + X_L^2}; \quad V = IZ$$

$$V = \sqrt{V_R^2 + V_L^2}$$

$$\tan \theta = \frac{\omega L}{R}$$

AC with LCR series circuit

Reactance: $X = X_L - X_C = \omega L - \frac{1}{\omega C}$

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

$$V^2 = V_R^2 + (V_L - V_C)^2$$

$$\tan \theta = \left(\frac{X_L - X_C}{R}\right) \text{ and } \cos \theta = \left(\frac{R}{Z}\right)$$

1. If $X_L > X_C$; then current lags behind the voltage.
2. If $X_L < X_C$; then current leads the voltage.
3. If $X_L = X_C$; then current and voltage are in same phase. This is called the case of resonance and resonant frequency is given by the condition

$$X_L = X_C$$

- Resonant frequency $f = \frac{1}{2\pi\sqrt{LC}}$

- In series resonance circuit,

a. Impedance is minimum; $Z = R$

b. Power factor; $\cos \theta = 1$

c. Current flowing is maximum; $I_{max} = \frac{V}{R}$

d. Circuit is resistive only.

- Series resonant circuit is called **acceptor** circuit.
- In parallel resonance circuit, at resonance current is minimum and impedance is maximum. Parallel resonance circuit is called **rejector** circuit.
- $I = I_0 \cos \theta$ is called wattful component of current.
- $I = I_0 \sin \theta$ is called wattless component of current because it does not contribute any power.

Choke coil

Choke coil is simply a coil having large inductance but a small resistance.

- It is used to control current in AC circuit.
- It is used in fluorescent tubes.
- Power factor of the coil is nearly zero i.e. power loss in circuit is minimum.

- It is a simple LR circuit with impedance,

$$Z = \sqrt{R^2 + \omega^2 L^2}$$

- Quality factor of a coil;

$$\text{Q. F.} = \frac{\omega L}{R} = \frac{2\pi f L}{R} = \frac{X_L}{R}$$

Transformer

It a device for converting high voltage into low voltage and vice-versa.

- It is based on the principle of mutual induction.
- It always works on AC.

It is of two types:

a. **Step up transformer:** It converts low voltage into high voltage. In this transformer number of turn in secondary is more than the no. of turn in primary.

b. **Step down transformer:** It converts high voltage into low voltage. In this transformer no. of turns in secondary is less than primary.

- The ratio of number of turns in secondary and primary is called turn ratio.

$$\text{Turn ratio: } \eta = \frac{n_s}{n_p}$$

- If E_p and E_s are alternating voltages; i_p and i_s the alternating currents across primary and secondary terminals respectively then:

$$\frac{E_s}{E_p} = \frac{i_p}{i_s} = \frac{n_s}{n_p} = n$$

Efficiency of transformer

$$\eta = \frac{\text{Output power}}{\text{Input power}}$$

$$\therefore \frac{P_{\text{out}}}{P_{\text{in}}} = \frac{E_s \cdot i_s}{E_p \cdot i_p}$$

- Efficiencies of the order of 99% can be easily achieved.
- In transformer frequency is not change.
- Transmission of power at high voltage is economical.